

Combinational Logic

CS211 Chapter 5

James YU

yujq3@sustech.edu.cn

Department of Computer Science and Engineering
Southern University of Science and Technology

Jul. 12, 2022




南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY

Combinational logic

- Logic circuits for digital systems:
 - combinational logic,
 - sequential logic (next lectures).
- *Combinational?*
 - Output determined by the combination of inputs.
 - Perform an operation specified by a set (combination) of Boolean functions.


Combinational logic

 - An interconnection of logic gates that
 - react to values of input signals,
 - produce output signal values,
 - n inputs from external sources, and
 - m outputs go to external destinations.



Combinational logic

 - Two representations of a combinational circuit:
 - 2^n possible input combinations: truth table, or
 - m outputs: m Boolean functions, each expressed with the n inputs.



Analysis of combinational logic


- Analysis of a combinational circuit: determine the function of the circuit.
 - Given logic diagram,
 - develop a set of Boolean functions, a truth table, an optional explanation of the circuit operation.
- If a function name or an explanation is given along the circuit, just verify if the given information is correct.

Analysis of combinational logic

- Obtain the output Boolean functions:
 - Label all gate outputs that are a function of only inputs, no other intermediate variables. Determine their Boolean functions.
 - Label all gates that are a function of inputs and the gates in the previous step. Determine their Boolean functions.
 - List output Boolean functions, squeeze the intermediate variables.

Analysis of combinational logic

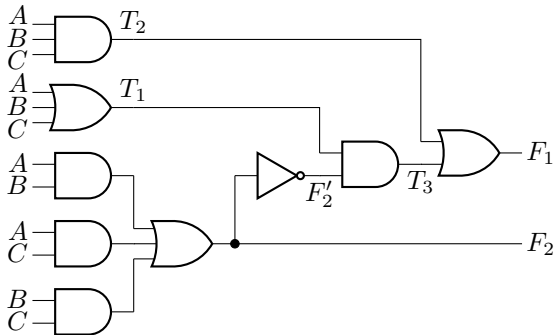
- Obtain the output Boolean functions:
 - Label all gate outputs that are a function of only inputs, no other intermediate variables. Determine their Boolean functions.



- $T_1 = A + B + C$.
- $T_2 = ABC$.
- $F_2 = AB + AC + BC$.

Analysis of combinational logic

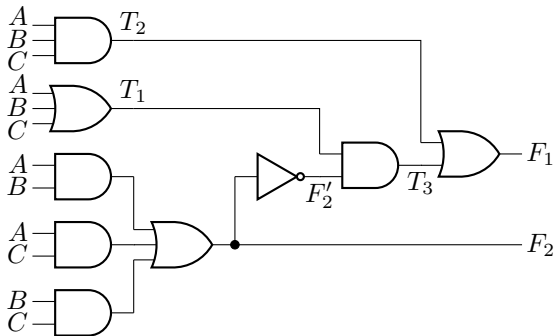- Obtain the output Boolean functions:
 - Label all gates that are a function of inputs and the gates in the previous step. Determine their Boolean functions.




- $T_3 = F'_2 + T_1.$

- $F_1 = T_2 + T_3.$

Analysis of combinational logic



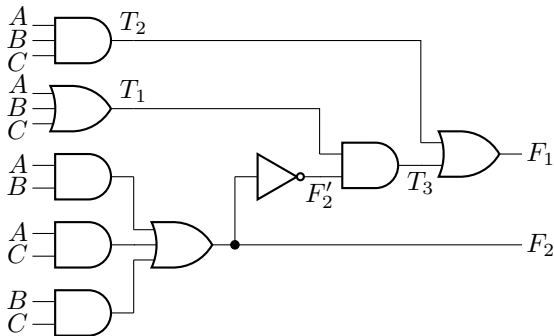- Obtain the output Boolean functions:
 - List output Boolean functions, squeeze the intermediate variables.



$$\begin{aligned} F_1 &= T_2 + T_3 \\ &= ABC + F_2' T_1 \\ &= ABC + \\ &\quad (AB + AC + BC)' \\ &\quad (A + B + C) \\ &= ABC + A'B'C + \\ &\quad AB'C' + A'BC' \end{aligned}$$

Analysis of combinational logic

- Truth table is simple with Boolean function
 - Determine the number of input variables. For n inputs, form the 2^n combinations from 0 to $2^n - 1$.
 - Label the outputs of the intermediate gates.
 - Obtain the truth table for these outputs.
 - Obtain the truth table for the remaining outputs.

A	B	C	F_2	F_2'	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Design of combinational logic

- Design of a combinational circuits: develop a logic circuit diagram or a set of Boolean functions.
 - From specification of the design objective
- Involves the following steps:
 - Determine required number of inputs and outputs.
 - Derive the truth table.
 - Obtain simplified Boolean function for each output.
 - Draw logic diagram and verify the correctness.

Design of combinational logic

- Example: Convert from BCD decimal code to excess-3 code.

Input BCD				Output Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

- Obviously, four inputs and four outputs
- And we already have the truth table
- Then the Boolean functions. How?
 - Remember K-maps?

Design of combinational logic

$$w = A + BC + BD$$

AB \ CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$x = B'C + B'D + BC'D' + CD'$$

AB \ CD	00	01	11	10
00		1	1	1
01	1			1
11	X	X	X	X
10		1	X	X

Design of combinational logic



$$y = CD + C'D'$$

AB \ CD	00	01	11	10
00	1		1	
01	1		1	
11	X	X	X	X
10	1		X	X


$$z = D'$$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X

Design of combinational logic

- We manipulate these Boolean functions to reuse common gates:
 - $w = A + BC + BD = A + B(C + D)$.
 - $x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$.
 - $y = CD + C'D' = CD + (C + D)'$.
 - $z = D'$.

Design of combinational logic

 


Combinational logic design with MSI circuits

- Since the introduction of MSI and LSI circuits, the traditional methods of logic design have largely been superseded.
 - Traditionally, the design engineer has developed a Boolean equation as the solution to a particular problem.
 - This function has then been minimised and implemented using SSI circuits.
- In practice, many combinational circuits may have a large number of inputs and outputs.
 - Consequently the use of truth tables in the design of such circuits is impractical.
- The development of MSI circuits has led to the technique of splitting a complex design into a number of sub-systems.


Multiplexer

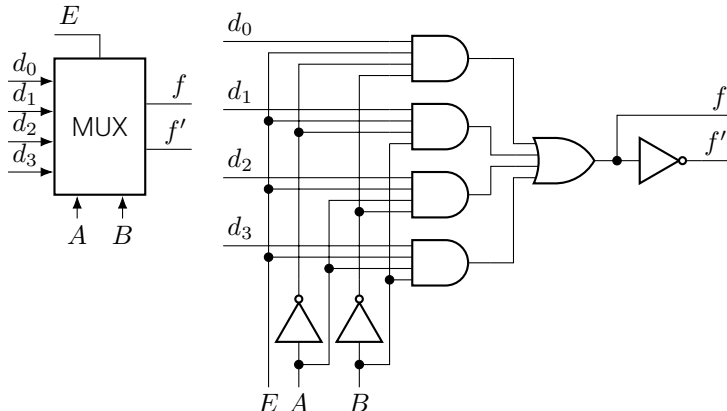- A multiplexer (MUX) selects 1-out-of- n lines where n is usually 2, 4, 8, or 16.
- A block diagram of a multiplexer having four input data lines d_0 , d_1 , d_2 , and d_3 and complementary outputs f and f' .




Multiplexer

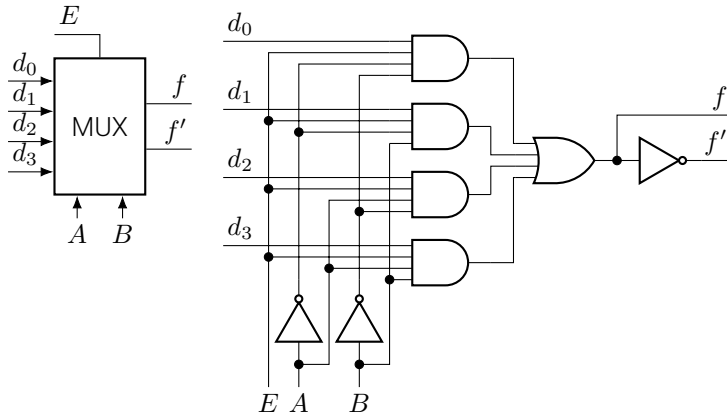- The device has two control or selection lines A and B and an enable line E .
- The characteristic equation of the multiplexer is
$$f = A'B'd_0 + A'Bd_1 + AB'd_2 + ABd_3.$$



Interconnecting multiplexers

 - Data within a digital system is normally processed in parallel form in order to increase the speed of operation.
- If the output of the system has to be transmitted over a relatively long distance then a parallel-to-serial conversion will take place.
- Example: An 8-bit word is presented in parallel at the data inputs.



Interconnecting multiplexers


- The principle of data selection can be extended to allow the selection of 1-out-of-64 lines.
 - Using nine 8-to-1 multiplexers arranged in two levels of multiplexing.
 - **How?**

Multiplexer as a Boolean function generator



- For a 4-to-1 MUX the characteristic equation is
$$f = A'B'd_0 + A'Bd_1 + AB'd_2 + ABd_3.$$
 - A and B are Boolean variables, applied at the select inputs, which can be factored out of any Boolean function of n variables.
 - The remaining $n - 2$ variables, referred to as the *residue variables*, can be formed into residue functions which can then be applied at the data inputs.
- Example: $f(A, B, C) = \sum(0, 1, 3, 4, 7).$

$A \backslash BC$	00	01	11	10
0	1	1	1	
1	1		1	

 


Multiplexer as a Boolean function generator




- Example: $f(A, B, C, D) = \sum(0, 1, 3, 4, 5, 9, 10, 11, 14, 15)$.

A	B	C	D	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
...				

 


Decoder

 - The basic function of an MSI decoder having n inputs is to select 1-out-of- 2^n output lines.
 - The selected output is identified either by a 1, when all other outputs are 0, or by a 0 when all other outputs are 1.




Decoder

 - It will be seen that the logic diagram of the basic decoder is identical to that of the basic demultiplexer.
 - Provided the data line is used to enable the decoder.
- The decoder may also be regarded as a minterm generator. Each output generates one minterm.



Decoder

 - If $A = B = C = D = 0$ the output 0 of the decoder is active low while all other outputs are 1.
- The decoder can generate the inverse of the 16 minterms.
- Example: $f(A, B, C, D) = \sum(0, 1, 5, 8, 10, 12, 13, 15)$.







Decoder network

- When a large decoding network is required it cannot be implemented in a single MSI package.
 - Mainly because of the large number of pins needed.
- The decoding range can be extended by interconnecting decoder chips. Two schemes:
 - *Tree decoding.*
 - *Coincident decoding.*

Decoder network

 


Decoder network

 

Encoder

 - An encoder performs the inverse operation to that of a decoder.
- Example: CPU master flag



- The encoder is designed to identify one, and only one, of the peripherals at any given instant.
 - In practice, there is nothing to prevent two or more peripherals requesting service at the same time.
 - To deal with this situation a system of priorities can be attached to the peripheral flags.

Encoder

- Example: Octal-to-binary encoder.

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- Eight inputs and three outputs connected with OR.



Encoder

- $x = D_4 + D_5 + D_6 + D_7$.
- $y = D_2 + D_3 + D_6 + D_7$.
- $z = D_1 + D_3 + D_5 + D_7$.
- Only one input can be active for one time.
 - D_3 and D_6 are 1 simultaneously: outputs $(111)_2 = 7$.
 - Encoder circuit must have priority: *Priority encoder*.

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	x	x	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Encoder



$$x = D_2 + D_3$$

$D_0D_1 \backslash D_2D_3$		D_2D_3			
		00	01	11	10
00	X	1	1	1	
01		1	1	1	
11		1	1	1	
10		1	1	1	


$$y = D_3 + D_1D_2'$$

$D_0D_1 \backslash D_2D_3$		D_2D_3			
		00	01	11	10
00	X	1	1		
01	1	1	1		
11	1	1	1		
10		1	1		



Encoder

 - $x = D_2 + D_3$.
- $y = D_3 + D_1 D_2'$.
- $V = D_0 + D_1 + D_2 + D_3$.




Digital comparator

- The usual problem for a comparator is the comparison of two multi-digit words such as $A = A_2A_1A_0$ and $B = B_2B_1B_0$.
 - Start from most to least significant bit.
 - $A = B$ if all bits are equal: $A_i = B_i$.
 - $x_i = A_iB_i + A'_iB'_i$.
- $A = B$ if $x_2x_1x_0 = 1$.
- $A > B$ if $A_2B'_2 + x_2A_1B'_1 + x_2x_1A_0B'_0 = 1$.
- $A < B$ if $A'_2B_2 + x_2A'_1B_1 + x_2x_1A'_0B_0 = 1$.


Digital comparator

 - The implementation of a 3-bit comparator is based on a single bit comparator.



- Using the equations developed in the last page, we can have a 3-bit comparator.

Digital comparator

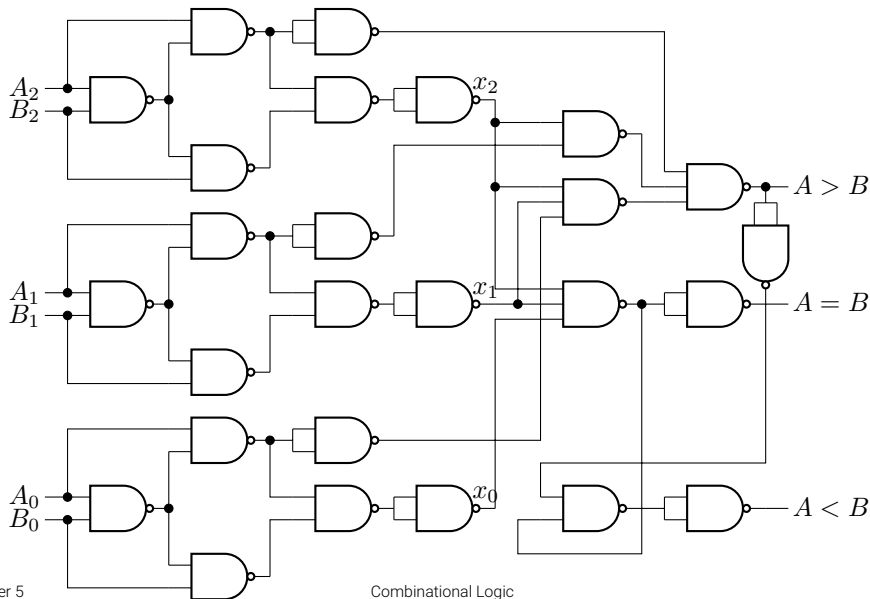

Exercise

- Design a combinational circuit with three inputs and one output.
 - The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise.
 - The output is 1 when the binary value of the inputs is an even number.

Exercise

- An 8×1 multiplexer has inputs A , B , and C connected to the selection inputs S_2 , S_1 , and S_0 , respectively. The data inputs I_0 through I_7 are as follows: $I_1 = I_2 = 0$; $I_3 = I_7 = 1$; $I_4 = I_5 = D$; and $I_0 = I_6 = D'$. Determine the Boolean function that the multiplexer implements.



Exercise

- A combinational circuit is defined by the equations

$$F_1(A, B, C) = AB + A'B'C'$$

$$F_2(A, B, C) = A + B + C$$

$$F_3(A, B, C) = A'B + AB'$$

Design a circuit which will implement these three equations using a decoder and NAND gates external to the decoder.