

A decorative graphic on the left side of the slide consists of a network of light blue lines and small circles, resembling a circuit board or a stylized tree structure, extending from the top to the bottom of the frame.

DIGITAL DESIGN

LAB10 SYNCHRONOUS SEQUENTIAL CIRCUIT


2022 SUMMER TERM

LAB10

- Synchronous sequential circuit
 - Latch
 - Flip Flop (key point of lab10)
 - The conversion between each other
- Practice

 4-2 PRIORITY-ENCODER IN LAB8

```
//4-2 priencoder
module encoder(
    input I0,
    input I1,
    input I2,
    input I3,
    output reg [1:0] Y
);
always @*
begin
    casex ({I3, I2, I1, I0})
        4'bxxx0: Y=2'b00;
        4'bxx01: Y=2'b01;
        4'bx011: Y=2'b10;
        4'b0111: Y=2'b11;
    endcase
end
endmodule
```




If there is no default and the case branch is incomplete, when the case branch is not listed in the case branch, the circuit state will remain unchanged, and then a latch will be generated to save the state.

LATCH

- The schematic of the synthesized design.
- LDCE: transparent Data Latch with Asynchronous Clear and Gate Enable

For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*

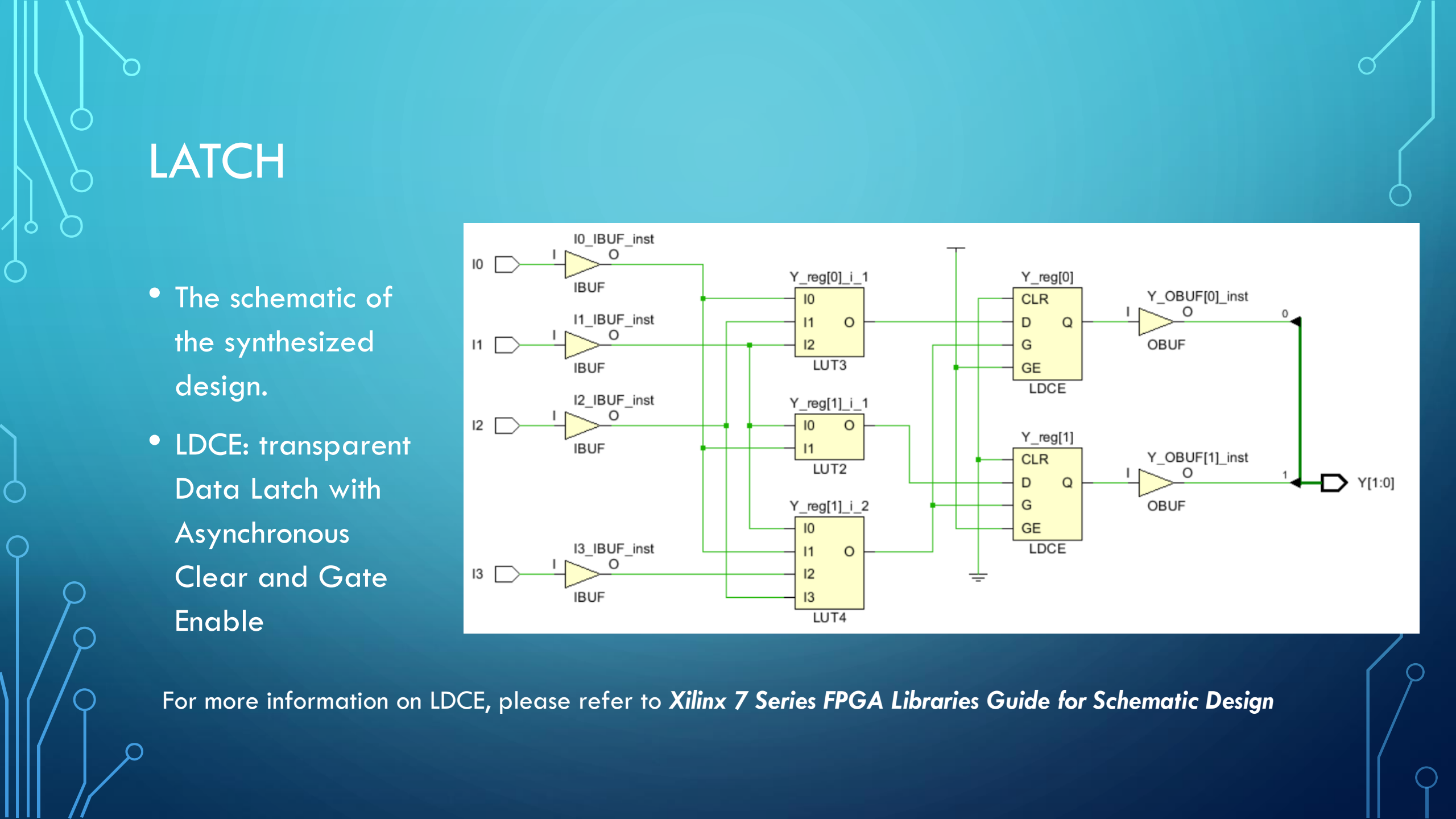- # LATCH
- The schematic of the synthesized design.
 - LDCE: transparent Data Latch with Asynchronous Clear and Gate Enable
-
- For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*



LATCH

- The schematic of the synthesized design.
- LDCE: transparent Data Latch with Asynchronous Clear and Gate Enable


For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*

```

module encoder(
    input I0,
    input I1,
    input I2,
    input I3,
    output reg [1:0] Y
);


always @*
begin
    casex({I3, I2, I1, I0})
        4'bxxx0: Y = 2'b00;
        4'bxx01: Y = 2'b01;
        4'bx011: Y = 2'b10;
        4'b0111: Y = 2'b11;
        default: Y = 2'b00;
    endcase
end
endmodule

```

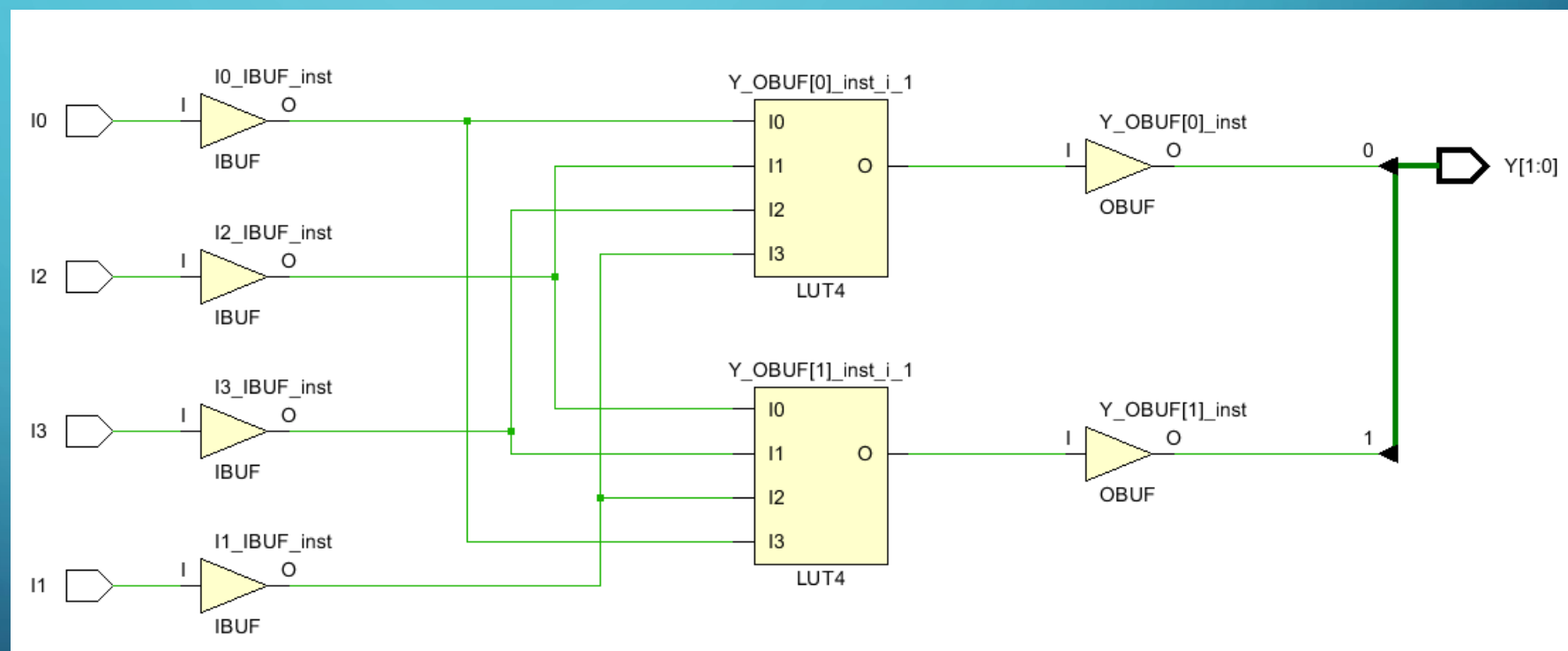

D LATCH


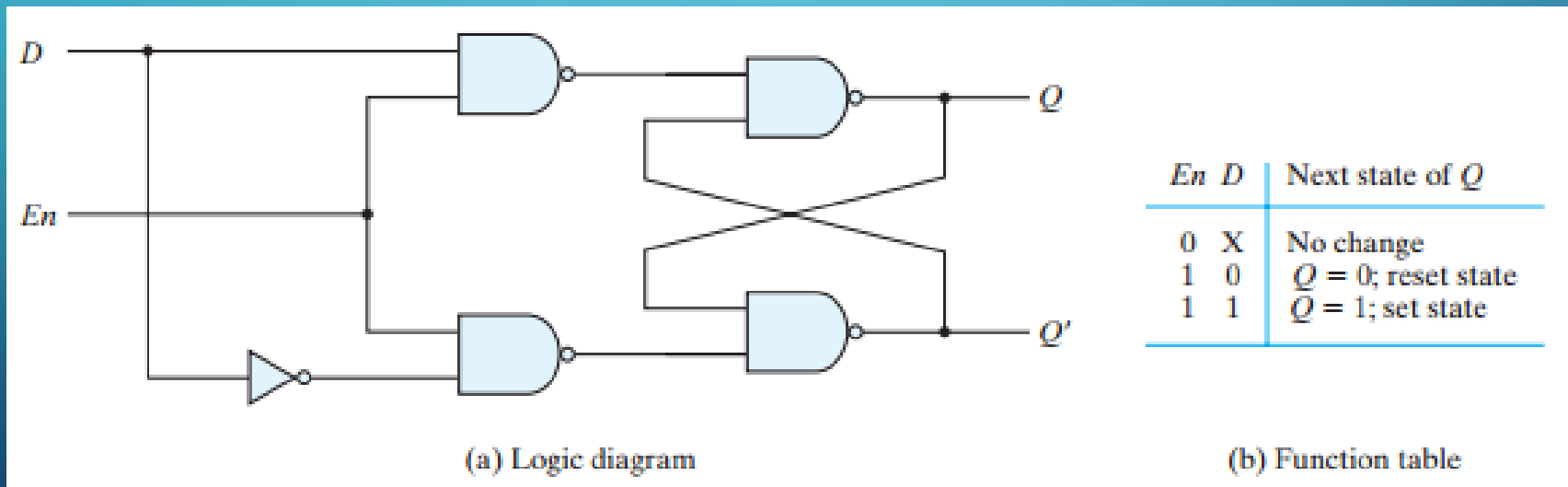
- Latch: the simplest binary memory elements, static device composed of gates. When the input changes, the output changes immediately.



D LATCH CONTINUED

- Schematic of RTL analysis
 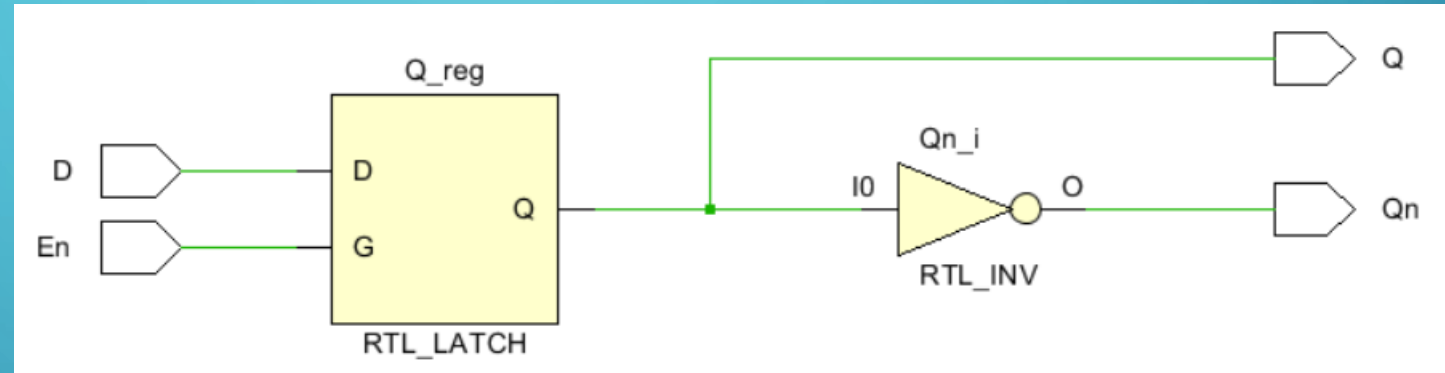
```
module D_Latch(  
  input En, D,  
  output reg Q,  
  output Qn  
);  
assign Qn = ~Q;  
always @*  
  if (En)  
    begin  
      Q = D;  
    end  
  else  
    Q = Q;  
endmodule
```




D LATCH CONTINUED

- Generate latch of multi-bit

```
module Latch_4bit(
    input [3:0] EN,
    input [3:0] D_4bit,
    output [3:0] Q_4bit,
    output [3:0] Qn_4bit
);
    D_Latch UUT3(.EN(EN[3]),.D(D_4bit[3]),.Q(Q_4bit[3]),.Qn(Qn_4bit[3]));
    D_Latch UUT2(.EN(EN[2]),.D(D_4bit[2]),.Q(Q_4bit[2]),.Qn(Qn_4bit[2]));
    D_Latch UUT1(.EN(EN[1]),.D(D_4bit[1]),.Q(Q_4bit[1]),.Qn(Qn_4bit[1]));
    D_Latch UUT0(.EN(EN[0]),.D(D_4bit[0]),.Q(Q_4bit[0]),.Qn(Qn_4bit[0]));
endmodule
```


```
Latch_4bit tb(
    .EN(EN),
    .D_4bit(D_4bit),
    .Q_4bit(Q_4bit),
    .Qn_4bit(Qn_4bit)
);
```
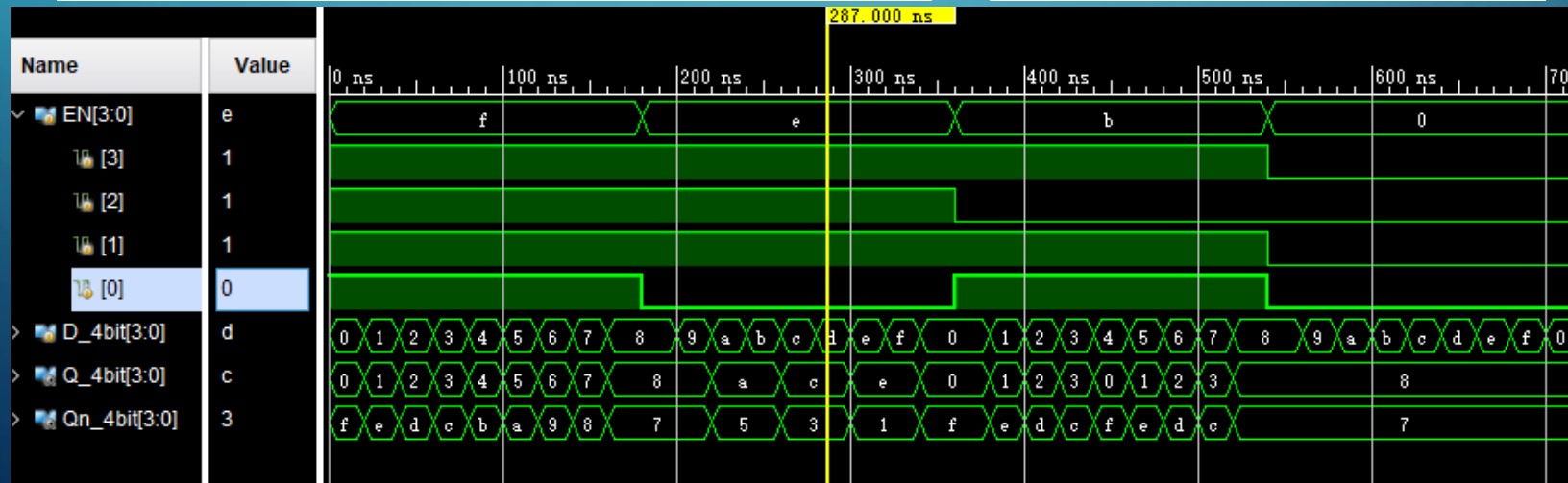
```
initial begin
    D_4bit = 4'b0000;
    EN = 4'b1111;
    repeat(8) #20 D_4bit = D_4bit + 1;
    #20 EN = 4'b1110;
    repeat(8) #20 D_4bit = D_4bit + 1;
    #20 EN = 4'b1011;
    repeat(8) #20 D_4bit = D_4bit + 1;
    #20 EN = 4'b0000;
    repeat(8) #20 D_4bit = D_4bit + 1;
    #20 $finish;
end
```



FLIP FLOP

 - The storage elements (memory) used in clocked sequential circuits are called *flipflops*.
- The most economical and efficient flip-flop constructed is the edge-triggered *D* flipflop, because it requires the smallest number of gates.




```
ve D_ff_from_latch (D_ff_from_latch.v) (2)
  ve DL_master : D_Latch (D_Latch.v)
  ve DL_slaver : D_Latch (D_Latch.v)
```

Figure for master-slave negative-edge triggered D flip-flop

FLIP FLOP CONTINUED

```
module DFF_from_Latch(  
    input CLK,  
    input D,  
    output Q  
);  
    wire Y;  
    D_Latch_2 DL_master(.EN(CLK),.D(D),.Q(Y));  
    D_Latch_2 DL_slave(.EN(~CLK),.D(Y),.Q(Q));  
endmodule
```
 
```
DFF_from_Latch tb0(  
    .CLK(CLK),  
    .D(D),  
    .Q(Q)  
);  
always #100 CLK = ~CLK;  
initial begin  
    #10 D = 1'b1;  
    #20 D = 1'b0;  
    #30 D = 1'b1;  
    #40 D = 1'b0;  
    #50 D = 1'b1;  
    #60 D = 1'b0;  
    #70 D = 1'b1;  
    #80 D = 1'b0;  
    #90 D = 1'b1;  
end
```



FLIP FLOP CONTINUED

- **classification**

- According to different logic functions: RS trigger, D trigger, JK Trigger and T trigger
- According to different trigger modes: level trigger, edge trigger and pulse trigger
- According to the different circuit structure: RS trigger and clock controlled trigger
- According to the principle of storing data: static trigger and dynamic trigger
- According to the physical components: bipolar flip flops and MOS flip flops


D FLIP FLOP

- $Q^{n+1} = D$

Clk	Q
↑	D
0	no change
1	no change
↓	no change

```

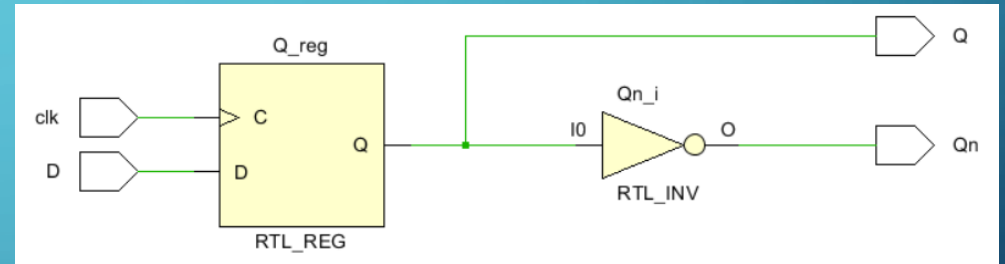module D_flipflop(
input clk,D,
output reg Q,
output Qn
);
always @(posedge clk)
begin
    Q <= D;
end
assign Qn = ~Q;
endmodule
    
```




JK FLIP FLOP(1)

- $Q^{n+1} = J\bar{Q}^n + \bar{K}Q^n$

J	K	Q^{n+1}
0	0	no change
0	1	0
1	0	1
1	1	$Q^{n'}$


JK Q^n	JK			
	00	01	11	10
0	0	0	1	1
1	1	0	0	1

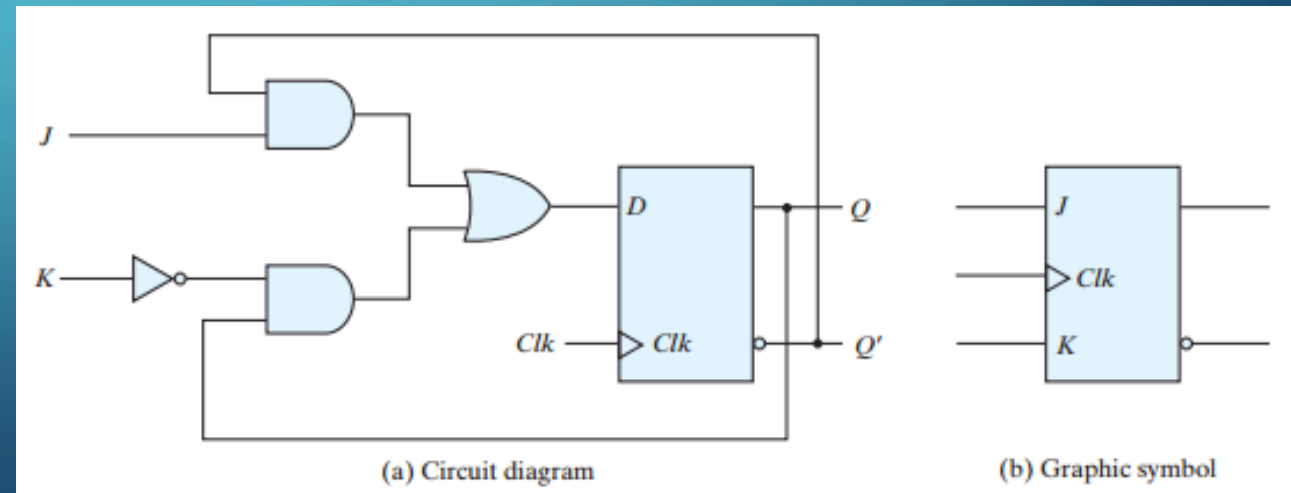

JK FLIP FLOP(2)

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

 
```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q,  
    output Qn  
);  
    assign Qn = ~Q;  
    always @(posedge Clk)  
    if({J, K} == 2'b10) //set  
    begin  
        Q <= 1'b1;  
    end  
    else if ({J, K} == 2'b01) //reset  
    begin  
        Q <= 1'b0;  
    end  
    else if ({J, K} == 2'b11) //reverse  
    begin  
        Q <= Qn;  
    end  
endmodule
```



USING JK FLIP FLOP TO IMPLEMENT D FLIP FLOP

- JK Flip-Flop: $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$
- D Flip-Flop: $Q^{n+1} = D = D\overline{Q}^n + DQ^n$

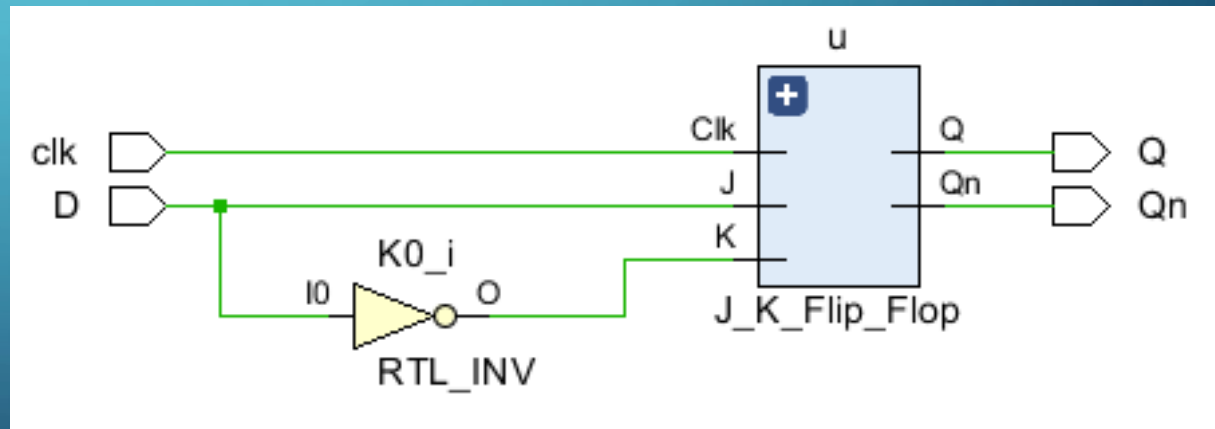
```
module D_Flip_Flop_JK(  
    input clk, D,  
    output Q, Qn  
);  
    J_K_Flip_Flop u(clk, D, ~D, Q, Qn);  
endmodule
```



T FLIP FLOP


- The T (toggle) flip-flop is a complementing flip-flop, which can be obtained from a JK flip-flop when inputs J and K are tied together.

T	Q^{n+1}
0	Q^n
1	$\sim Q^n$

 

```
module T_Flip_Flop(  
    input Clk, T,  
    output reg Q,  
    output Qn  
);  
    assign Qn = ~Q;  
    always @(posedge Clk)  
        case (T)  
            1'b1: Q <= Qn;  
        endcase  
endmodule
```

```
module T_Flip_Flop_JK(  
    input T, Clk,  
    output Q,  
    output Qn  
);  
    J_K_Flip_Flop u(Clk, T, T, Q, Qn);  
endmodule
```

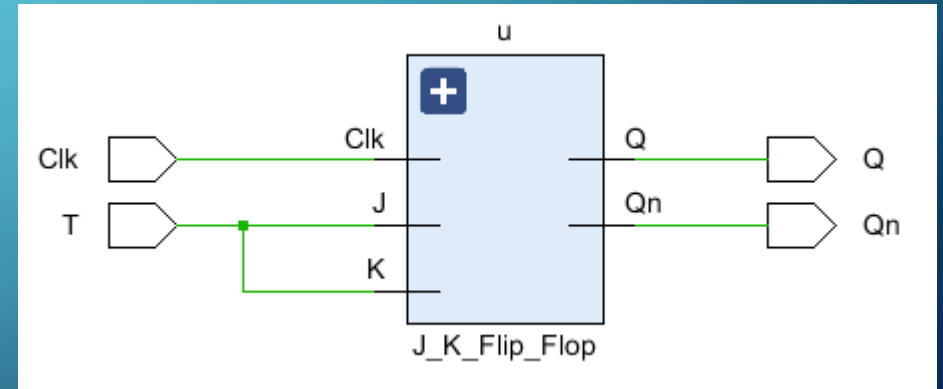

PRACTICE 1

- Try to construct a T Flip Flop with primitive gates.
 - Do the design and verify the function of your design.
 - Create the constraint file, do the synthesis and implementation, generate the bitstream file and program the device, then test on the EGO1 develop board.

PRACTICE 2


$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

- Can this JK flip-flop work when doing simulation?
- Try to use it to implement a T flip-flop, do the design, create constraint file, generate the bitstream file and program the device.
- Can the T flip-flop work when doing simulation? Explain the reason.

```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q, Qn  
);  
always @(posedge Clk)  
    if({J, K} == 2'b10) //set  
        begin  
            {Q, Qn} <= 2'b10;  
        end  
    else if ({J, K} == 2'b01) //reset  
        begin  
            {Q, Qn} = 2'b01;  
        end  
    else if ({J, K} == 2'b11) //reverse  
        begin  
            Q <= Qn;  
            Qn <= Q;  
        end  
end  
endmodule
```

TIPS:

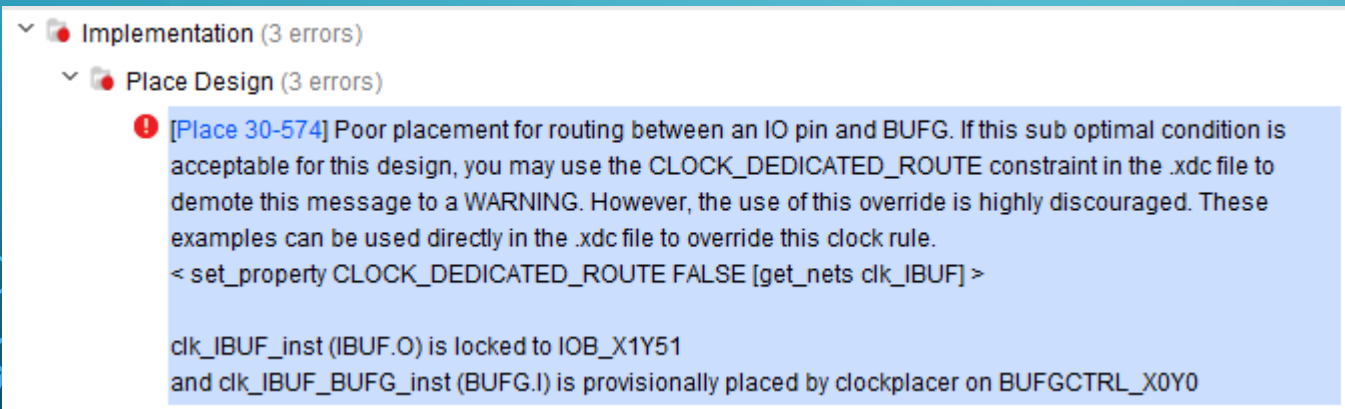- Constraints: if you want to use IO pin as clock, you should use the CLOCK_DEDICATED_ROUTE constraint in the .xdc file to demote the Error message to a WARNING.



```
set_property PACKAGE_PIN Y9 [get_ports clk]
set_property PACKAGE_PIN W9 [get_ports D]
set_property PACKAGE_PIN K17 [get_ports Q]
set_property PACKAGE_PIN L13 [get_ports Qn]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports Qn]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_IBUF]
```

A red arrow points from the first line of code to the error message in the previous image. The last line of code is highlighted with a red box.