



DIGITAL DESIGN

LAB9 COMBINATORIAL CIRCUIT3

2022 SUMMER TERM

LAB8

- Combinational circuit(3)
 - Multiplexer
 - Demultiplexer
- Practice

MULTIPLEXER


- a **Multiplexer** (or **mux**) is a device that selects one of several input signals and forwards the selected input into a single line.
- A multiplexer of 2^n inputs has n select lines, which are used to select which input line to be sent to the output.
- Multiplexers are mainly used to increase the amount of data that can be sent over the network within a certain amount of time and bandwidth. A multiplexer is also called a **data selector**.
- Multiplexers can also be used to implement Boolean functions of multiple variables.

MULTIPLEXER

$$Y = m_0.D_0 + m_1.D_1 + m_2.D_2 + m_3.D_3$$

selection input		output
s1	s0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

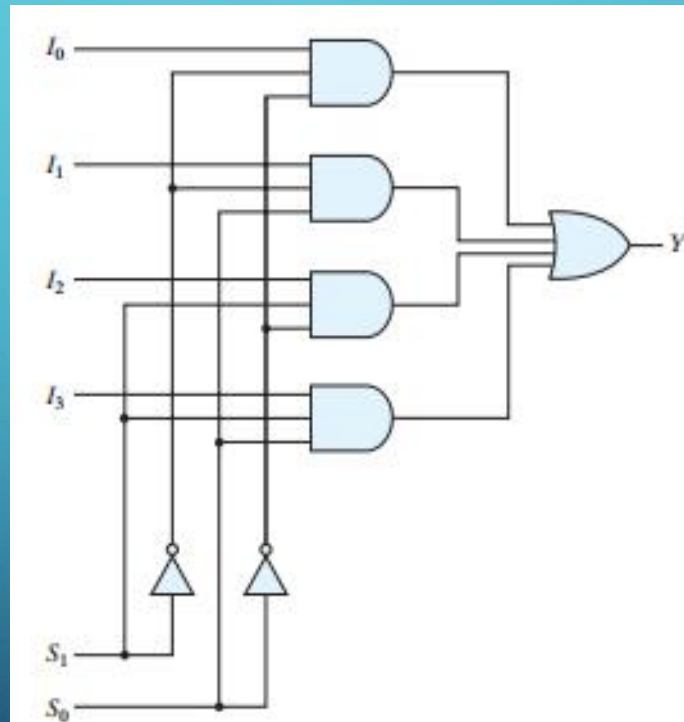function table for 4-to-1-line
multiplexer



```
module multiplexer(  
    input w,  
    input x,  
    input y,  
    input z,  
    input [1:0] s, //select  
    output reg o  
);  
always @*  
begin  
    case (s)  
        2'b00: o = w;  
        2'b01: o = x;  
        2'b10: o = y;  
        2'b11: o = z;  
    endcase  
end  
endmodule
```


MULTIPLEXER

$$Y = m_0 \cdot D_0 + m_1 \cdot D_1 + m_2 \cdot D_2 + m_3 \cdot D_3$$

selection input		output
s1	s0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

function table for 4-to-1-line
multiplexer

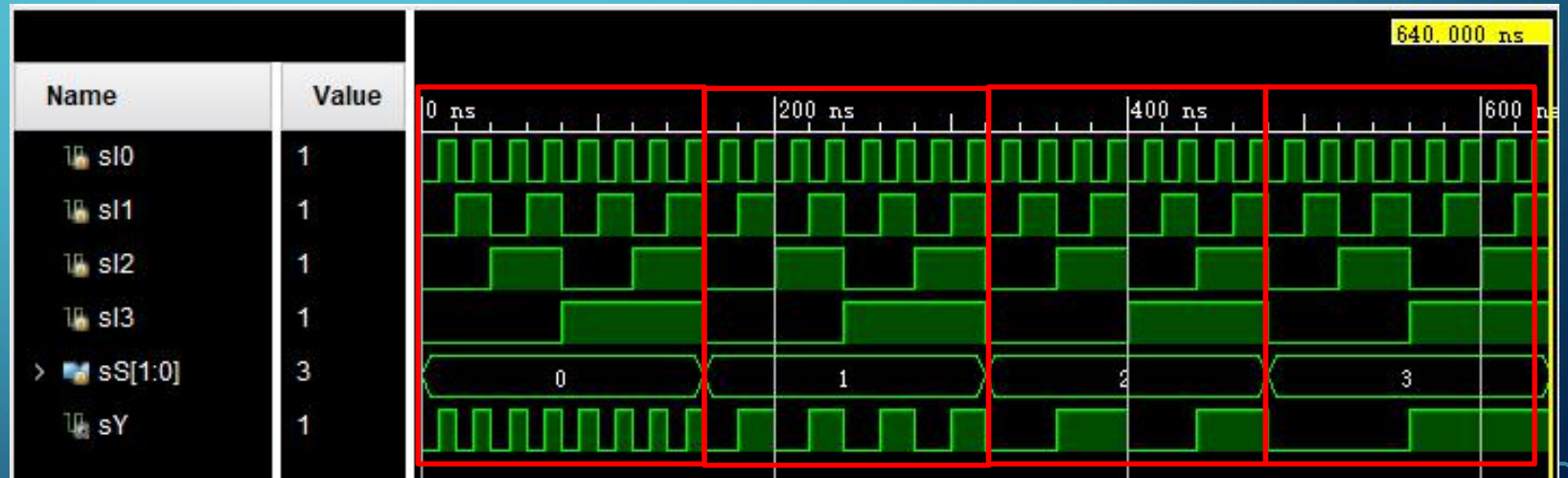
```
module multiplexer_tb();
    reg sI0, sI1, sI2, sI3;
    reg [1:0]sS;
    wire sY;
    multiplexer u(sI0, sI1, sI2, sI3, sS, sY);
    initial
    begin
        {sS, sI3, sI2, sI1, sI0} = 6'b000000;
        repeat(63) #10 {sS, sI3, sI2, sI1, sI0} = {sS, sI3, sI2, sI1, sI0} + 1;
        #10 $finish;
    end
endmodule
```



MULTIPLEXER(74151)



Logic diagram

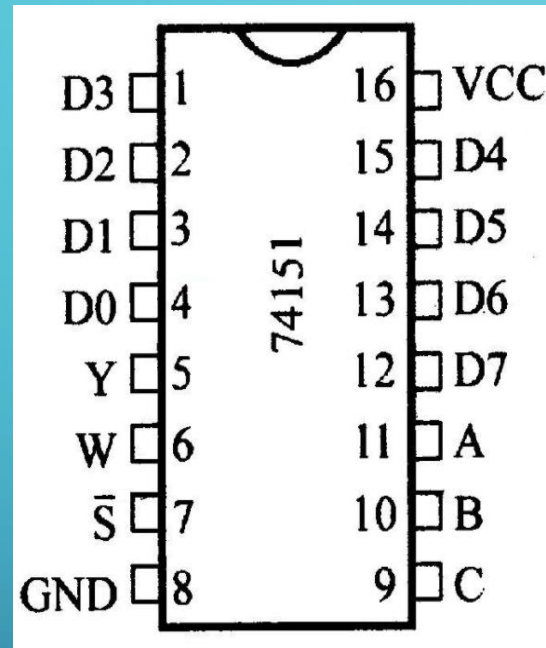

Pin diagram



Physical photo

- **74151**: 8-to-1-line multiplexer
- 1 strobe input (low level effective)
- 3 select lines
- 8 data inputs
- Y is the data output
- W is the reverse code of data output

MULTIPLEXER(74151) CONTINUED


inputs				output	
EN	S2	S1	S0	Y	W
1	X	X	X	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

function table for 74151

```

module multiplexer74151( EN, S2, S1, S0, D7, D6,
D5, D4, D3, D2, D1, D0, Y, W);
    input EN, S2, S1, S0, D7, D6, D5,
        D4, D3, D2, D1, D0;
    output reg Y;
    output W;
    always @*
    if (~EN)
        case ({S2, S1, S0})
            3'b000: Y = D0;
            3'b001: Y = D1;
            3'b010: Y = D2;
            3'b011: Y = D3;
            3'b100: Y = D4;
            3'b101: Y = D5;
            3'b110: Y = D6;
            3'b111: Y = D7;
        endcase
    else
        Y = 1'b0;
    assign W=~Y;
endmodule

```

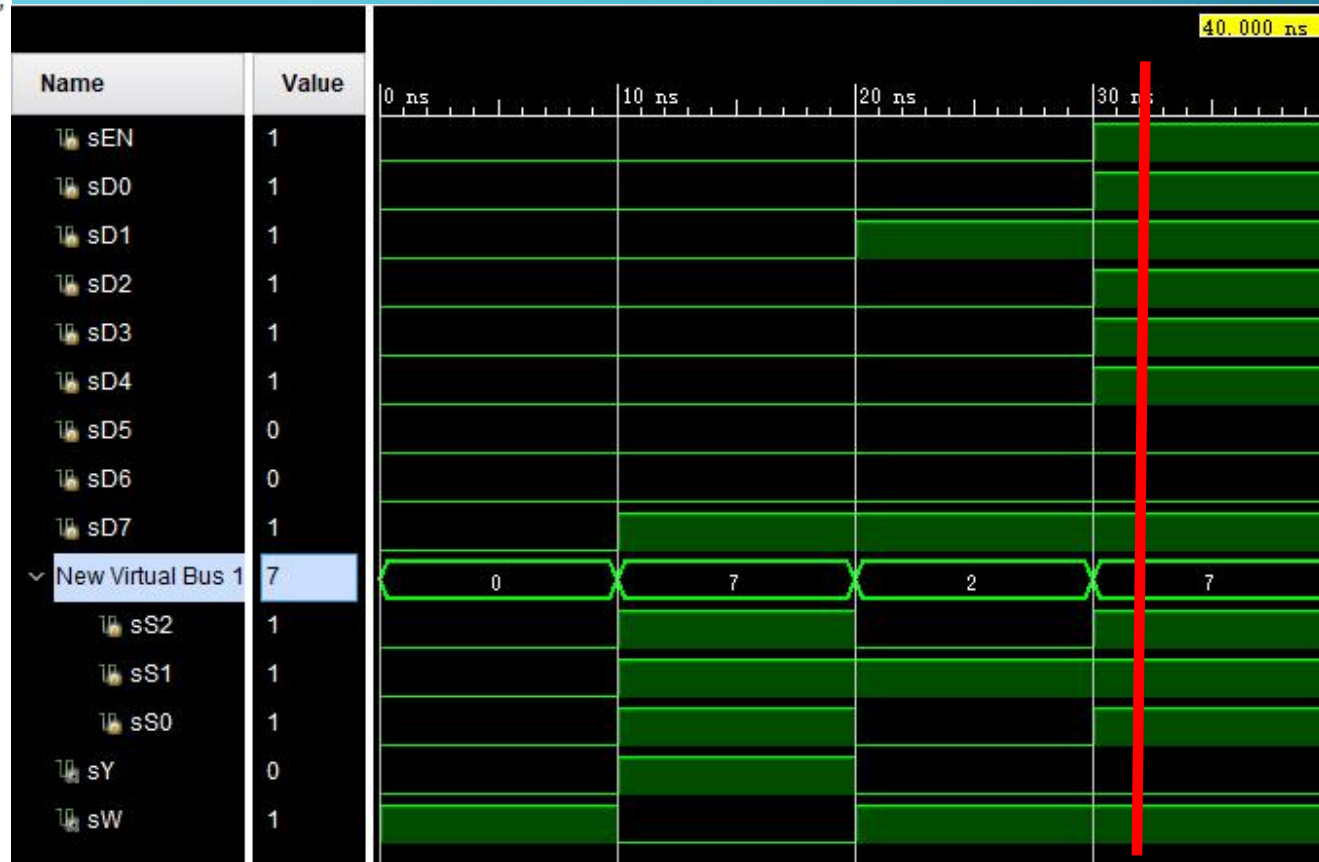


MULTIPLEXER(IMPLEMENT BOOLEAN FUNCTIONS-1)

- Use 74151 implement the following logic function.

$$\begin{aligned}F(A, B, C) &= \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}B + BC \\&= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}BC + ABC + \overline{A}BC \\&= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}BC + ABC \\&= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC\end{aligned}$$

$$= m_0.1 + m_1.0 + m_2.1 + m_3.1 + m_4.1 + m_5.0 + m_6.0 + m_7.1$$
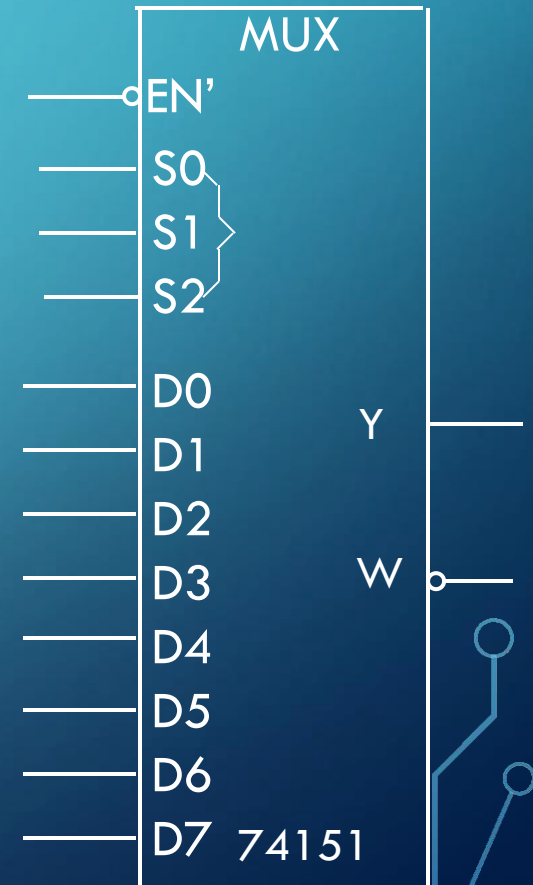
$$Y = m_0.D_0 + m_1.D_1 + m_2.D_2 + m_3.D_3 + m_4.D_4 + m_5.D_5 + m_6.D_6 + m_7.D_7$$



MULTIPLEXER(IMPLEMENT BOOLEAN FUNCTIONS-2)

$$F(A, B, C) = \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}B + BC$$

```
module multiplexer74151( EN, S2, S1, S0, D7, D6, D5, D4, D3, D2, D1, D0, Y, W );
    input EN, S2, S1, S0, D7, D6, D5, D4, D3, D2, D1, D0;
    output reg Y;
    output W;
    always @*
    if (~EN)
        case ({S2, S1, S0})
            3'b000: Y = D0;
            3'b001: Y = D1;
            3'b010: Y = D2;
            3'b011: Y = D3;
            3'b100: Y = D4;
            3'b101: Y = D5;
            3'b110: Y = D6;
            3'b111: Y = D7;
        endcase
    else
        Y = 1'b0;
    assign W=~Y;
endmodule
```

```
module fun_a_b_c(input A,B,C, output F );
    assign F=( (~A)&(~C) ) | ( (~B)&(~C) ) | ((~A)&B) | (B&C) ;
endmodule
```

$$F(A, B, C) = m_0.1 + m_1.0 + m_2.1 + m_3.1 + m_4.1 + m_5.0 + m_6.0 + m_7.1$$

```
module fun_a_b_c_use_mux(input A,B,C, output F);
    wire sen,sd7,sd6,sd5,sd4,sd3,sd2,sd1,sd0;
    wire snf;

    assign {sen,sd7,sd5,sd4,sd3,sd2,sd1,sd0}= 9'b0_1001_1101;

    multiplexer74151 u74151(.EN(sen),
        .S2(A),.S1(B),.S0(C),
        .D7(sd7),.D6(sd6),.D5(sd5),.D4(sd4),.D3(sd3),.D2(sd2),.D1(sd1),.D0(sd0),
        .Y(F),.W(snf));

endmodule
```

MULTIPLEXER(IMPLEMENT BOOLEAN FUNCTIONS-3)

```
timescale 1ns / 1ps
//////////////////////////////////////////...
module fun_abc_sim();
  reg sa, sb, sc;
  wire sf, sf_mux;
  fun_a_b_c uf(.A(sa),.B(sb),.C(sc),.F(sf));
  fun_a_b_c_use_mux uf_mux(.A(sa),.B(sb),.C(sc),.F(sf_mux));
  /*...*/
  initial
  begin
    {sa, sb, sc} = 3'b000;
    repeat(7)
    begin
      #100 {sa, sb, sc} = {sa, sb, sc} + 1;
      $display($time, "{sa, sb, sc}=%d_%d_%d sf=%d sf_mux=%d", sa, sb, sc, sf, sf_mux);
    end
    #100 $finish();
  end
endmodule
```

$$F(A, B, C) = \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}B + BC$$

```
100{sa, sb, sc}=0_0_1 sf=1 sf_mux=1
200{sa, sb, sc}=0_1_0 sf=0 sf_mux=0
300{sa, sb, sc}=0_1_1 sf=1 sf_mux=1
400{sa, sb, sc}=1_0_0 sf=1 sf_mux=1
500{sa, sb, sc}=1_0_1 sf=1 sf_mux=1
600{sa, sb, sc}=1_1_0 sf=0 sf_mux=0
700{sa, sb, sc}=1_1_1 sf=0 sf_mux=0
$finish called at time : 800 ns : File "D:/xilinx_wor
```

DE-MULTIPLEXER


- a **De-multiplexer** (or **De-mux**) is a device taking a single input signal and selecting one of many data-output-lines, which is connected to the single input.

selection input		output			
S1	S0	Y3	Y2	Y1	Y0
0	0	0	0	0	D
0	1	0	0	D	0
1	0	0	D	0	0
1	1	D	0	0	0

function table of 1-to-4 de-multiplexer
D is the data input


```
module demultiplexer(  
    input D,  
    input [1:0] S,  
    output reg Y0,  
    output reg Y1,  
    output reg Y2,  
    output reg Y3  
)  
always@*  
begin  
    case (S)  
        2'b00: {Y3, Y2, Y1, Y0}={1'b0, 1'b0, 1'b0, D};  
        2'b01: {Y3, Y2, Y1, Y0}={1'b0, 1'b0, D, 1'b0};  
        2'b10: {Y3, Y2, Y1, Y0}={1'b0, D, 1'b0, 1'b0};  
        2'b11: {Y3, Y2, Y1, Y0}={D, 1'b0, 1'b0, 1'b0};  
    endcase;  
end  
endmodule
```

```
module demultiplexer_tb();  
    reg [1:0] sS;  
    reg sD;  
    wire sY0, sY1, sY2, sY3;  
    demultiplexer u(sD, sS, sY0, sY1, sY2, sY3);  
    initial  
    begin  
        {sD, sS} = 3'b000;  
        repeat(7) #10 {sD, sS} = {sD, sS}+1;  
        #10 $finish;  
    end  
endmodule
```

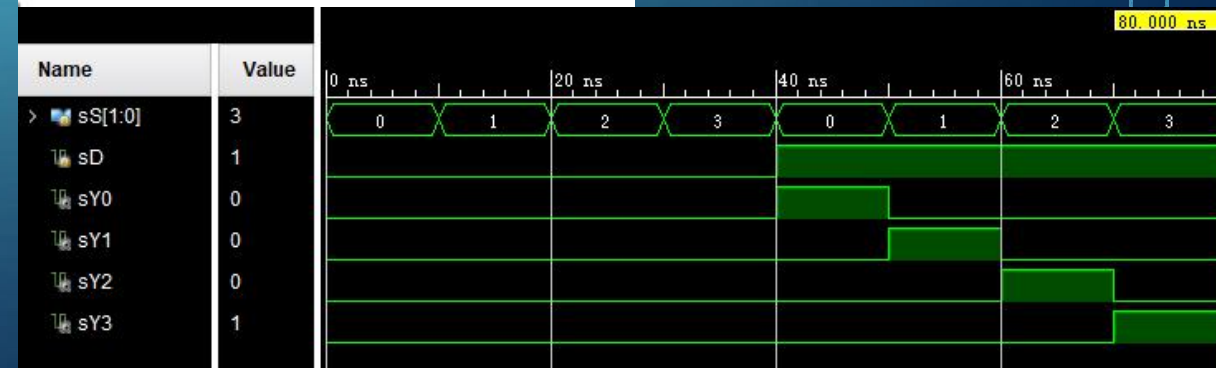

PRACTICE 1

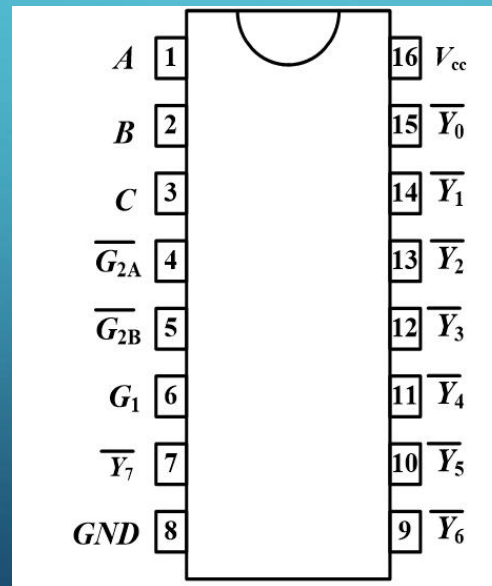- Is there any relationship between Decoder and De-mux?
- Please try to implement a 1-8 De-mux by using Decoder 74138
- Tips: Use $\overline{G_{2A}}$ pin as the data input of De-mux



G1	G2A'	G2B'	C	B	A	Y0'	Y1'	Y2'	Y3'	Y4'	Y5'	Y6'	Y7'
0	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	1	X	X	X	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	0	1	1	0	1	1	1	1	1	1
1	0	0	0	1	0	1	1	0	1	1	1	1	1
1	0	0	0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	0	0	1	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1	1	1	1	0	1	1
1	0	0	1	1	0	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0

truth table for 74138 decoder

PRACTICE 2

- Use 74151 (8-to-1-line multiplexer) realize the following logic function

$$Y = A'B'C'D' + BC'D + A'C'D + A'BCD + ACD$$

- Do the design
- Verify the function of your design
- Create the constraint file, do the synthetic and implementation, generate the bitstream file and program the device, then test on EGO1.