

A decorative graphic on the left side of the slide, consisting of a network of white lines and small circles on a blue gradient background, resembling a circuit board or a tree structure.

# DIGITAL DESIGN

VERILOG SUMMARY

2022 SUMMER TERM

# LAB14

- Verilog
  - Summary
  - Synthesizable vs Non-Synthesizable

# VERILOG SUMMARY(1)

- **Design-Under-Test vs Test-Bench**

- **Structured design**

- (top module , instance modules)

- **Block**

- Combinational, Sequential

- **Statement**

- continuous assignment
- Unblock assignment vs block assignment
- If else, case, loop

- **Variable vs Constant**

- reg vs wire
- Splicing { , }
- Number system

# VERILOG SUMMARY(2)

- **Non-Synthesizable Verilog** which is **NOT suggested** to use in your design
  - initial
  - Task, function
  - System task : \$display, \$monitor, \$strobe, \$finish
  - fork... join
  - UDP

# VERILOG SUMMARY(3)

- **Suggested**

- Using an asynchronous reset to make your system go to initial state
- Using case instead of embedded 'if-else' to avoid unwanted priority and longer delay

- **NOT suggested**

- Embedded 'if-else'
- Two different edge trigger for one always block
- (!!!) **a signal/port is assigned in more than one always block** (it won't report error while synthesized but its behavior maybe wrong after synthesize)
- Mix-use blocking assignment and non-blocking assignment in one always block

# DUT VS TESTBENCH

- DUT is a designed module with input and output ports
  - While do the design, non-synthesizable grammar means can't be convert to circuit, is NOT suggested!
  - DUT may be a top module using structured design which means the sub module is instanced and connected in the top module
- Testbench is used for test DUT with NO input and output ports
  - Instance the DUT, bind its ports with variable, set the states of variable which bind with inputs and check the states of variable which bind with outputs
  - Testbench is NOT part of Design, it only runs in FPGA/ASIC EDA, so the un-synthesizable grammar can be used in testbench



# MODULE (STRUCTURED LEVEL VS TESTBENCH)

```
module multiplexer_153(out,c0,c1,c2,c3,a,b,g1n);
input c0,c1,c2,c3;
input a,b;
input g1n;
output reg [3:0] out;

always @(*)
if(1'b0==g1n)
    case({b,a})
        2'b00:out=4'b1110;
        2'b01:out=4'b1101;
        2'b10:out=4'b1011;
        2'b11:out=4'b0111;
    endcase
else
    out = 4'b1111;
endmodule
```

```
module multiplexer_153_2(out1,out2,c10,c11,c12,c13,a1,b1,g1n,
    c20,c21,c22,c23,a2,b2,g2n);
input c10,c11,c12,c13,a1,b1,g1n,c20,c21,c22,c23,a2,b2,g2n;
output out1,out2;

multiplexer_153 m1(
    .g1n(g1n),
    .a(a1),
    .b(b1),
    .c0(c10),
    .c1(c11),
    .c2(c12),
    .c3(c13),
    .out(out1)
);


multiplexer_153 m2(
    .g1n(g2n),
    .a(a2),
    .b(b2),
    .c0(c20),
    .c1(c21),
    .c2(c22),
    .c3(c23),
    .out(out2)
);

endmodule
```

```
module lab3_df_sim( );
    reg simx,simy;
    wire simq1,simq2,simq3;
    lab3_df u_df(
        .x(simx), .y(simy), .q1(simq1), .q2(simq2), .q3(simq3) );

    initial
    begin
        simx=0;
        simy=0;
        #10
        simx=0;
        simy=1;
        #10
        simx=1;
        simy=0;
        #10
        simx=1;
        simy=1;
    end
endmodule
```

# FSM AND VERILOG

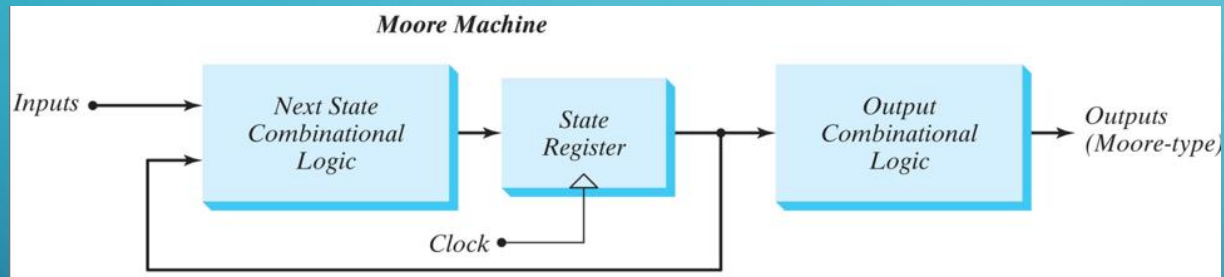

```
`timescale 1ns / 1ps
///////////////////////////////////////////////////
module moore_2b(input clk,rst_n,x_in,output[1:0] state,next_state);
    reg [1:0] state,next_state;
    parameter S0=2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
    always @(posedge clk,negedge rst_n) begin
        if(~rst_n)
            state <= S0;
        else
            state <= next_state;
    end
    always @(state,x_in) begin
        case(state)
            S0: if(x_in) next_state = S1; else next_state = S0;
            S1: if(x_in) next_state = S2; else next_state = S1;
            S2: if(x_in) next_state = S3; else next_state = S2;
            S3: if(x_in) next_state = S0; else next_state = S3;
        endcase
    end
end
endmodule
```



# MODULE DESIGN

- Gate level
  - Implementation from the perspective of gate-level structure of the circuit, Using gates as components, connecting pins of gates
  - using logical and bitwise operators or original primitive(not , or , and , xor , xnor ..)
- Data streams
  - Implementation from the perspective of data processing and flow
  - Using continuous assignment, pay attention to the correlation between signals, the difference between logical and bitwise operators
- Behavior Level
  - Implementation from the perspective of the Behavior of Circuits
  - Implemented in the always statement block
  - The variable which is assigned in the always block Must be Reg type.

# IF – ELSE IN BEHAVIOR MODELING

'if else' block can represent the priority between signals

From the overall structure, from top to bottom, priority decreases in turn

```
module updown_counter(D,CLK,CR,LD,UP,Q)
input [3:0]D;
input CLK,CR,LD,UP;
output reg [3:0] Q;

always @(posedge CLK )
if(!CR)
Q=0;
else if(!LD)
Q=D;
else if(UP)
Q=Q+1;
else
Q=Q-1;
endmodule
```



NOTIC:


- 1) If there is no 'else' branch in the statement, latches will be generated while doing the synthesis.
- 2) Nested 'if-else' is NOT suggested, 'case' is suggested as an alternative.

# CASE IN BEHAVIOR MODELING

case	0	1	x	z
0	1	0	0	0
1	0	1	0	0
x	0	0	1	0
z	0	0	0	1

```
module decoder(cIn,data,addr);
input cIn;
input [1:0] addr;
output reg [3:0] data;

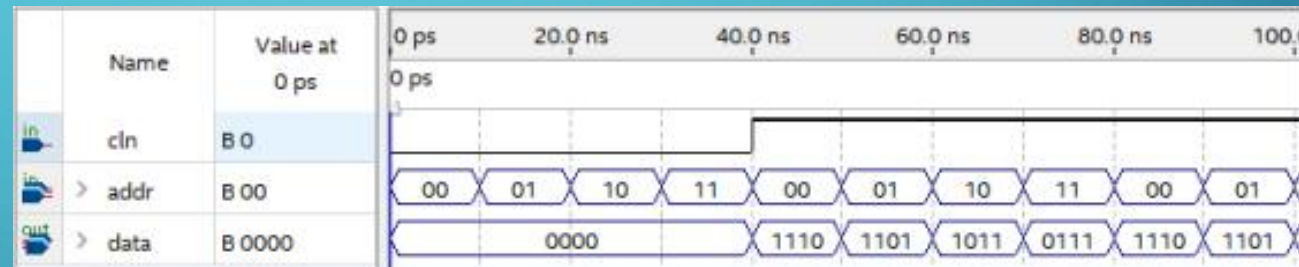always @(cIn or addr )
begin
if(0==cIn)
data=4'b0000;
else
case(addr)
2'b00:data=4'b1110;
2'b01:data=4'b1101;
2'b10:data=4'b1011;
2'b11:data=4'b0111;
endcase
end
endmodule
```




## NOTIC:

Without defining default branches and NOT all situations is cleared under the “case”, latches will be generated while doing the synthesis.

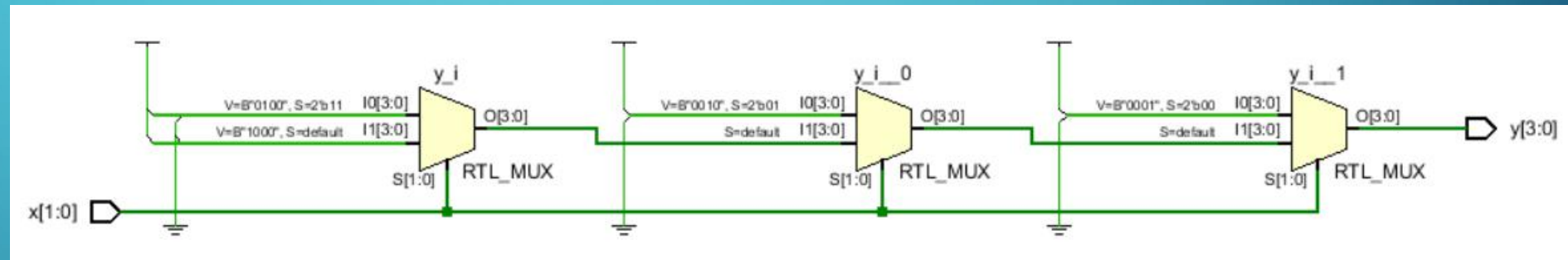
# VERILOG ( BE CAREFUL WITH EMBEDDED IF-ELSE )

- Embedded 'if-else' circuit brings priority and more latency compared to 'case'

```
always @*
  if( 2'b00 == x)
    y = 4'b0001;
  else if( 2'b01 == x)
    y = 4'b0010;
  else if( 2'b11 == x)
    y = 4'b0100;
  else
    y = 4'b1000;
```


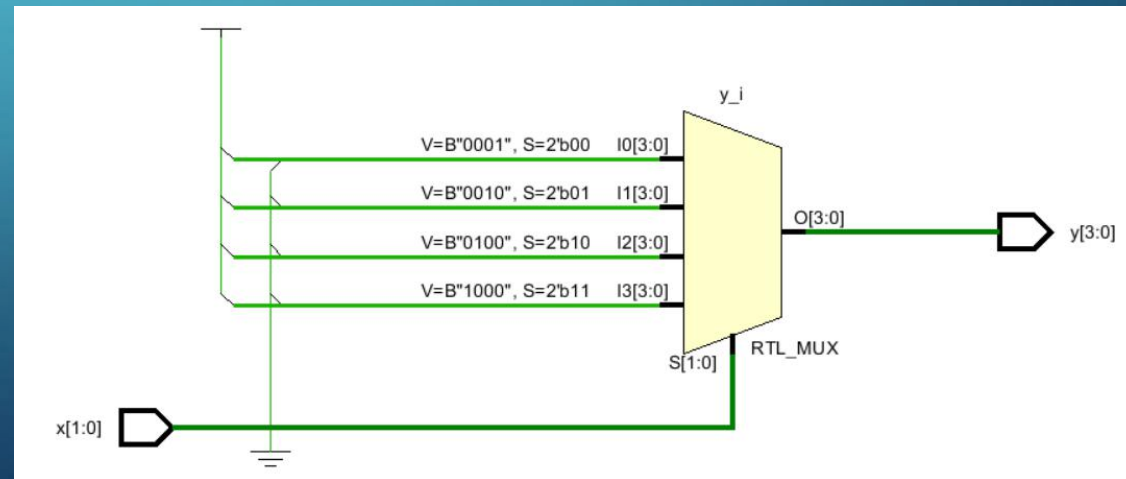
```
always @*
  case(x)
    2'b00: y=4'b0001;
    2'b01: y=4'b0010;
    2'b10: y=4'b0100;
    2'b11: y=4'b1000;
  endcase
```



# LOOP IN BEHAVIOR MODELING

- Loop is NOT used much in design, for its comprehensiveness is not very good.
- Loop is most often used in testbench to specify signal behavior:

```
repeat(12)
  begin
    Cin = 1'b0;
    Cin = #40000 1'b1;
    # 40000;
  end
```



# STATEMENT

- Assignment

- Continuous assign (MUST to a wire variable)

- assign A = 1'b0 ;            //A MUST be defined as a **wire**

- Block assign(used in initial or always block, MUST to a reg variable, usually in combinational block)

- always @ \*

- A = 1'b0;            //A MUST be defined as a **reg**

- initial

- A = 1'b0;            //A MUST be defined as a **reg**

- Un-block assign (used in initial or always block, MUST to a reg variable , usually in sequential block)

- always @(posedge clk)

- A <= 1'b0 ;            //A MUST be defined as a **reg**



# CONSTANT(1)

- Expression

- `<bit width>'<numerical system expression><number in the numerical system >`
  - numerical system expression
    - B / b : Binary
    - O / o : Octal
    - D / d : decimal
    - H / h : hexadecimal
- `'<numerical system expression><number in the numerical system >`
  - The default value of bit width is based on the machine-system(at least 32 bit)
- `<number>` : default in decimal
  - The default value of bit width is based on the machine-system(at least 32 bit)

# CONSTANT(2)

- x( uncertain state) and z (High resistivity state)
  - The default value of a wire variable is Z before its assignment
  - The default value of a reg variable is X before its assignment
- negative value
  - Minus sign must be ahead of bit-width
    - -4'd3 (is ok) while 4'd-3 is illegal
- underline
  - Can be used between number but can NOT be in the bit width and numerical system expression
    - 8'b0011\_1010 (is ok) while 8'\_b\_0011\_1010(is illegal)

# CONSTANT(3)

- Parameter (symbolic constants)
  - Used for improve the Readability and maintainability
  - Declare an identifier on a constant
  - Parameter `p1=expression1,p2=expression2,..;`

# VARIABLE (1)

- Variable

- Changeable while process

```
wire a;  
wire [7:0] b;  
wire [4:1] c,d;
```

- Wire

- Net
  - Can 't store info, must be driven (such as continuous assignment)
  - The input and output port of module is wire by default
  - Can NOT be the type of left-hand side of assignment in initial or always block

# VARIABLE (2)

- Reg

- **MUST** be the type of left-hand side of assignment in initial or always block
- The default initial value of reg is an indefinite value X. Reg data can be assigned positive values and negative values.
- When a reg data is an operand in an expression, its value is treated as an unsigned value, that is, a positive value.
- For example, when a 4-bit register is used as an operand in an expression, if the register is assigned -1. When performing operations in an expression. It is considered to be a complement representation of + 15 (- 1)

# WIRE VS REG

```
module sub_wr();  
  input reg in1,in2;  
  output out1;  
  output out2;  
endmodule
```

Error: Port in1 is not defined  
Error: Non-net port in1 cannot be of mode input  
Error: Port in2 is not defined  
Error: Non-net port in2 cannot be of mode input

```
module sub_wr(in1,in2,out1,out2);  
  input in1,in2;  
  output out1;  
  output reg out2;  
  
  assign in1 = 1'b1;  
  
  initial begin  
    in2 = 1'b1;  
  end  
endmodule
```

Error: procedural assignment to a non-register in2 is not permitted, left-hand side should be reg/integer/time/genvar

```
23 module test_wire_reg(  
24   );  
25   wire i1,i2;  
26   reg o1,o2;  
27   sub_wr s1(i1,i2,o1,o2);  
28 endmodule  
29  
30 module sub_wr(in1,in2,out1,out2);  
31   input in1,in2;  
32   output out1;  
33   output reg out2;  
34
```

[Synth 8-685] variable 'o1' should not be used in output port connection [test\_wire\_reg.v:27]



# MEMORY

- Memory can be seen as a set of registers with the same bit width.

Modeling memory by building arrays of reg variables, and addressing each unit of the array by array index

- Definition:

```
reg [n-1:0] memory name [m-1:0];    // there are m unit in memory, the size of each unit in the memory is n .
```

- Notes:

- A n-bit register can be assigned in an assignment statement, but a full memory CAN NOT.
- If you need to read and write a storage unit in memory, you must specify the address of the unit in memory.


```
reg [2:0] Mema [4:0];  // define a memory named Mema which has 5 memory units, each with a bit width of 3 bits.
```

```
Mema [1]= 3'b101;    // assign 3'b101  to Mema [1] unit in Mema
```
 
# MEMORY (DEMO)

```
module test(
    A, C0, C1, C2
);
    input [2:0] A;
    output [1:0] C0, C1, C2;
    reg[1:0] B [2:0];
    assign {C0, C1, C2} = {B[0], B[1], B[2]};
    always @(A)
    if(A)
    begin
        B[0] = 2'b11;
        B[1] = 2'b10;
        B[2] = 2'b01;
    end
    else
    begin
        B[0] = 2'b00;
        B[1] = 2'b00;
        B[2] = 2'b00;
    end
endmodule
```

```
module test(
    A, C0, C1, C2
);
    input [2:0] A;
    output [1:0] C0, C1, C2;
    reg[1:0] B [2:0];
    assign {C0, C1, C2} = {B[0], B[1], B[2]};
    always @(A)
    if(A)
    begin
        {B[0], B[1], B[2]} = 6'b011011;
        /*B[0] = 2'b11;
        B[1] = 2'b10;
        B[2] = 2'b01;*/
    end
    else
    begin
        {B[0], B[1], B[2]} = 6'b0;
        /*B[0] = 2'b00;
        B[1] = 2'b00;
        B[2] = 2'b00;*/
    end
endmodule
```



# OPERATOR(1)

highest priority	! ~
	* / %
	+ -
	<< >>
	< <= > >=
	== != === !==
	&
	^ ^~
	&&
lowest priority	? :

- Bit splicing operator { }

multiple data or bits of data are separated by commas in order, then using braces to splice them as a whole.

Such as: { a, B[1:0], w, 2'b10 } // Equivalent to { a, B[1], B[0], w, 1'b1, 1'b0 }

- Repetition can be used to simplify expressions

{ 4 {w} } // Equivalent to { w, w, w, w }


{ b, {2 {x, y} } } // Equivalent to { b, x, y, x, y }

# OPERATOR(2)

When numeric values are used for conditional judgment, non-zero values represent logical truth and zero values represent logical false.


```
module test_bool(A,C);
input [2:0]A;
output reg [2:0]C;

 always @(A )
begin
if(A)
C=2'b11;
else
C=2'b00;
end
endmodule
```



```
module test_bool(A,C);
input [2:0]A;
output reg [2:0]C;

 always @(A )
begin
if(A==1)
C=2'b11;
else
C=2'b00;
end
endmodule
```




# TIPS ON PROJECT(1)

- Using button on the developing board, notice the sharking of button while it is pressed and released.
- Avoid assigning to a variable in several always block, or it would cause conflicts
- Notice on the sensitive list of always block :
  - Suggested: '\*' is suggested in combinational logic
  - NOT suggested:
    - (posedge clk, negedge clk) // there is no corresponding component in FPGA
    - (posedge in1) is not suggested to find a posedge of an input signal


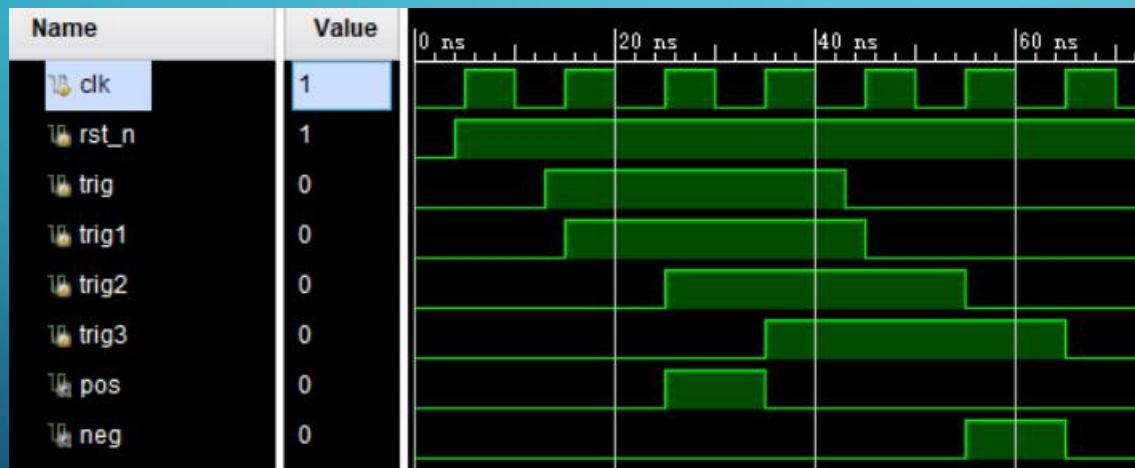
# TIPS ON PROJECT(2)

To find the posedge or negedge of input signal 'trig'  
Following method is suggested





# TIPS ON VIVADO (ADD INTRAL SIGNAL TO WAVEFORM)

