

# Arithmetic Circuits

CS211 Chapter 8

James YU

yujq3@sustech.edu.cn

Department of Computer Science and Engineering  
Southern University of Science and Technology

Jul. 26, 2022



南方科技大学  
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY

# Arithmetic circuits

- One important aspect of digital design not dealt with in earlier lectures is the design and implementation of arithmetic circuits.
  - Various information-processing jobs are carried out by digital computers.
  - Arithmetic operations are among the basic functions of a digital computer.

# Addition

- Addition of two binary digits is the most basic arithmetic operation.
  - $0 + 0 = 0$ ,
  - $0 + 1 = 1$ ,
  - $1 + 0 = 1$ ,
  - $1 + 1 = 10$ .
  - The higher significant bit of this result is called the *carry*.
- A combinational circuit that performs the addition of two bits as described above is called a *half-adder*.
- The addition operation involves three bits — the *augend bit*, *addend bit*, and the *carry bit* and produces a sum result as well as carry.
- The combinational circuit performing this type of addition operation is called a *full-adder*.



# Half-adder

- As described above, a half-adder has two inputs and two outputs.
- Let the input variables augend and addend be designated as  $A$  and  $B$ , and output functions be designated as  $S$  for sum and  $C$  for carry.


Input variables		Output variables	
$A$	$B$	$S$	$C$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- It can be seen that the outputs  $S$  and  $C$  functions are similar to Exclusive-OR and AND functions, respectively.



# Half-adder

- $S = A \oplus B$ ,
- $C = AB$ .

 

# Full-adder

- A combinational circuit of full-adder performs the operation of addition of three bits — the augend, addend, and previous carry  $X$ , and produces the outputs sum and carry.


Input variables			Output variables	
$X$	$A$	$B$	$S$	$C$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full-adder

$X \backslash AB$	00	01	11	10
0		1		1
1	1		1	


$X \backslash AB$	00	01	11	10
0			1	
1		1	1	1

 - $S = X'A'B + X'AB' + XA'B' + XAB,$
- $C = AB + BX + AX.$


 
# Full-adder

- It can also be implemented with two half adders and one OR gate, as shown below.




$$\begin{aligned} S &= B \oplus (X \oplus A) = B'(XA' + X'A) + B(XA' + X'A)' \\ &= B'(XA' + X'A) + B(XA + X'A') = XA'B' + X'AB' + XAB + X'A'B. \\ C &= B(XA' + X'A) + XA = XA'B + X'AB + XA \end{aligned}$$


 
# Binary adder

- A binary adder is a digital circuit that produces the arithmetic sum of two binary numbers.
- It can be constructed with full adders connected in cascade, with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- Addition of  $n$ -bit numbers requires a chain of  $n$  full adders or a chain of one-half adder and  $n - 1$  full adders.
  - Below shows the interconnection of four full-adder (FA) circuits to provide a four-bit binary ripple carry adder.




# Binary adder



- $1011 + 0011 = 1110$ .

Subscript $i$	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

 


# Binary adder

- The four-bit adder is a typical example of a standard component.
- It can be used in many applications involving arithmetic operations.
- Observe that the design of this circuit by the classical method would require a truth table with  $2^9 = 512$  entries, since there are nine inputs to the circuit.
- By using an iterative method of cascading a standard function, it is possible to obtain a simple and straightforward implementation.
 
# Carry propagation




- The addition of two binary numbers in parallel implies that all the bits of the augend and addend are available for computation at the same time.
- As in any combinational circuit, the signal must propagate through the gates before the correct output sum is available in the output terminals.
  - The total propagation time is equal to the propagation delay of a typical gate, times the number of gate levels in the circuit.
  - In this regard, consider output  $S_3$ . Inputs  $A_3$  and  $B_3$  are available as soon as input signals are applied to the adder.
  - However, input carry  $C_3$  does not settle to its final value until  $C_2$  is available from the previous stage.



# Carry propagation


- The carry propagation time is an important attribute of the adder because it limits the speed with which two numbers are added.
  - Since all other arithmetic operations are implemented by successive additions, the time consumed during the addition process is critical.
- A solution is to increase the complexity of the equipment in such a way that the carry delay time is reduced.
- The most widely used technique employs the principle of *carry lookahead logic*.

# Carry propagation

 

- Consider this full-adder circuit:
  - $P_i = A_i \oplus B_i$ ,
  - $G_i = A_i B_i$ .
- The output sum and carry can respectively be expressed as
  - $S_i = P_i \oplus C_i$ ,
  - $C_{i+1} = G_i + P_i C_i$ .
- $G_i$  is called a *carry generator*.  $P_i$  is called a *carry propagator*.

# Carry propagation

 

- We now write the Boolean functions for the carry outputs of each stage and substitute the value of each  $C_i$  from the previous equations.



$C_0$  = input carry,

$$C_1 = G_0 + P_0C_0,$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1G_0 + P_1P_0C_0,$$

$$C_3 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0.$$

# Carry propagation

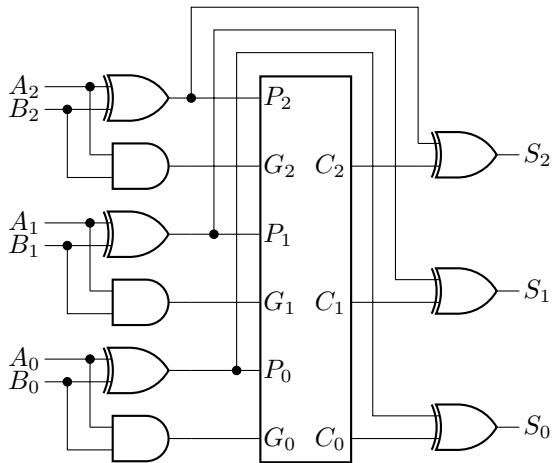 



# Subtraction

- Subtraction is the other basic function of arithmetic operations of information-processing tasks of digital computers.
  - $0 - 0 = 0$ ,
  - $0 - 1 = 1$  with borrow of 1,
  - $1 - 0 = 1$ ,
  - $1 - 1 = 0$ .
  - The first, third, and fourth operations produce a subtraction of one digit, but the second operation produces a difference bit as well as a *borrow* bit.
- A combinational circuit that performs the subtraction of two bits as described above is called a *half-subtractor*.
- the subtraction operation involves three bits — the *minuend* bit, *subtrahend* bit, and the *borrow* bit, and produces a different result as well as a borrow.
- The combinational circuit that performs this type of subtraction operation is called a *full-subtractor*.




# Half-subtractor

- As described above, a half-subtractor has two inputs and two outputs.
- Let the input variables minuend and subtrahend be designated as  $X$  and  $Y$ , and output functions be designated as  $D$  for difference and  $B$  for borrow.

Input variables		Output variables	
$X$	$Y$	$D$	$B$
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

- $D = X \oplus Y$ ,
- $B = X'Y$ .

 

# Full-subtractor

- A combinational circuit of full-subtractor performs the operation of subtraction of three bits – the minuend, subtrahend, and borrow  $Z$  generated from the subtraction operation of previous significant digits and produces the output difference and borrow.


Input variables			Output variables	
$X$	$Y$	$Z$	$D$	$B$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

# Full-subtractor

$X \backslash AB$	00	01	11	10
0		1		1
1	1		1	

$X \backslash AB$	00	01	11	10
0		1	1	1
1			1	

 - $D = X'Y'Z + X'YZ' + XY'Z' + XYZ$ ,
- $B = X'Z + X'Y + YZ$ .




# Binary subtractor

- The subtraction of unsigned binary numbers can be done most conveniently by means of complements.
  - The subtraction  $A - B$  can be done by taking the 2's complement of  $B$  and adding it to  $A$ .
  - The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits.
  - The 1's complement can be implemented with inverters, and a 1 can be added to the sum through the input carry.
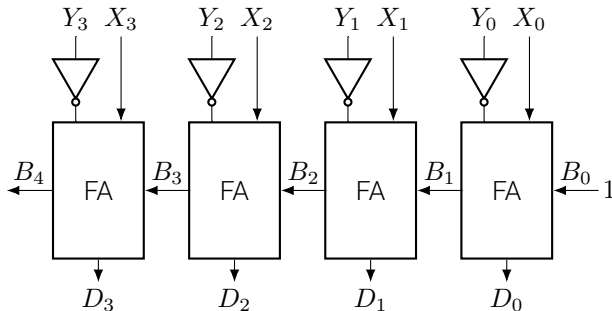
# Binary subtractor

- The circuit for subtracting  $A - B$  consists of an adder with inverters placed between each data input  $B$  and the corresponding input of the full adder.





# Binary subtractor

- It is worth noting that binary numbers in the signed-complement system are added and subtracted by the same basic addition and subtraction rules as are unsigned numbers.
- Therefore, computers need only one common hardware circuit to handle both types of arithmetic.



# Overflow



- When two numbers with  $n$  digits each are added and the sum is a number occupying  $n + 1$  digits, we say that an overflow occurred.
  - When the addition is performed with paper and pencil, an overflow is not a problem, since there is no limit by the width of the page to write down the sum.
- Overflow is a problem in digital computers because the number of bits that hold the number is finite and a result that contains  $n + 1$  bits cannot be accommodated by an  $n$ -bit word.
  - For this reason, many computers detect the occurrence of an overflow, and when it occurs, a corresponding flip-flop is set that can then be checked by the user.
- The detection of an overflow after the addition of two binary numbers depends on **whether the numbers are considered to be signed or unsigned**.
  - When two unsigned numbers are added, an overflow is detected from the end carry out of the most significant position.
  - When two signed numbers are added, the sign bit is treated as part of the number and the end carry does not indicate an overflow.

# Overflow

- An overflow may occur if the two numbers are both positive or negative.

carries:	0	1
+70	0	1000110
+80	0	1010000
+150	1	0010110
<hr/>		
carries:	1	0
-70	1	0111010
-80	1	0110000
-150	0	1101010

- If the carry out of the sign bit position is taken as the sign bit of the result, then the nine-bit answer so obtained will be correct.
- But since the answer cannot be accommodated within eight bits, we say that an overflow has occurred.


# Overflow

- An overflow condition can be detected by observing the carry into the sign bit position and the carry out of the sign bit position.
- If these two carries are not equal, an overflow has occurred.**

carries:	0	1	
+70	0	1000110	
+80	0	1010000	
+150	1	0010110	
<hr/>			
carries:	1	0	
-70	1	0111010	
-80	1	0110000	
-150	0	1101010	

- If the two carries are applied to an exclusive-OR gate, an overflow is detected when the output of the gate is equal to 1.

# Overflow

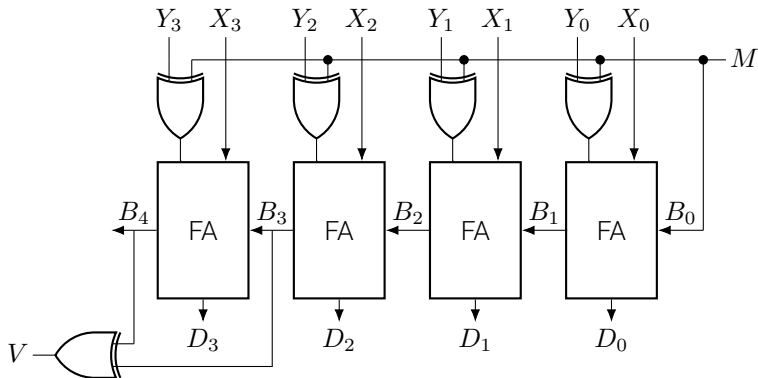

# Decimal adder

- Computers or calculators that perform arithmetic operations directly in the decimal number system represent decimal numbers in binary coded form.
- An adder for such a computer must employ arithmetic circuits that accept coded decimal numbers and present results in the same code.
- Consider the arithmetic addition of two decimal digits in BCD, together with an input carry from a previous stage.
  - Since each input digit does not exceed 9, the output sum cannot be greater than  $9 + 9 + 1 = 19$ , the 1 in the sum being an input carry.
  - Suppose we apply two BCD digits to a four-bit binary adder. The adder will form the sum in binary and produce a result that ranges from 0 through 19.



## Decimal adder


- When the binary sum is equal to or less than  $1001$ , the result is a valid BCD code.
- When the binary sum is greater than  $1001$ , we obtain an invalid BCD representation. The addition of binary 6 ( $0110$ ) to the binary sum converts it to the correct BCD representation and also produces an output carry as required.

$K$	$Z_8$	$Z_4$	$Z_2$	$Z_1$	$C$	$S_8$	$S_4$	$S_2$	$S_1$
0	1	0	1	0	1	0	0	0	0
0	1	0	1	1	1	0	0	0	1
0	1	1	0	0	1	0	0	1	0
0	1	1	0	1	1	0	0	1	1
0	1	1	1	0	1	0	1	0	0
0	1	1	1	1	1	0	1	0	1
1	0	0	0	0	1	0	1	1	0
1	0	0	0	1	1	0	1	1	1
1	0	0	1	0	1	1	0	0	0
1	0	0	1	1	1	1	0	0	1


 
# Decimal adder

- $C = K + Z_8Z_4 + Z_8Z_2$ .
- When  $C = 1$ , it is necessary to add 0110 to the binary sum and provide an output carry for the next stage.



# Binary multiplier

- Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers.
- The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit.
- Each such multiplication forms a partial product. Successive partial products are shifted one position to the left.


$$\begin{array}{r} \phantom{A_1 B_1} \phantom{A_1 B_0} \phantom{A_0 B_1} \phantom{A_0 B_0} \\ \phantom{A_1 B_1} \phantom{A_1 B_0} \phantom{A_0 B_1} B_1 \phantom{B_0} \\ \phantom{A_1 B_1} \phantom{A_1 B_0} \phantom{A_0 B_1} A_1 \phantom{A_0} \\ \hline \phantom{A_1 B_1} \phantom{A_1 B_0} A_0 B_1 \phantom{A_0 B_0} \\ \phantom{A_1 B_1} A_1 B_0 \phantom{A_0 B_0} \\ \hline C_3 \phantom{C_2} C_2 \phantom{C_1} C_1 \phantom{C_0} \end{array}$$


 
# Binary multiplier



$$\begin{array}{r}
 \begin{array}{cc}
 B_1 & B_0 \\
 A_1 & A_0 \\
 \hline
 A_0 B_1 & A_0 B_0 \\
 A_1 B_1 & A_1 B_0 \\
 \hline
 C_3 & C_2 & C_1 & C_0
 \end{array}
 \end{array}$$



# Binary multiplier

- A combinational circuit binary multiplier with more bits can be constructed in a similar fashion.
  - A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier.
  - The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product.